
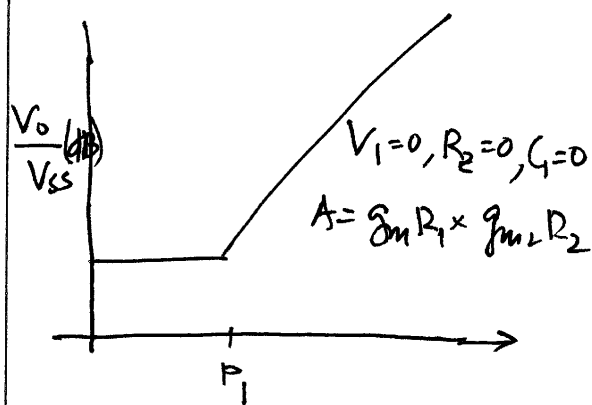
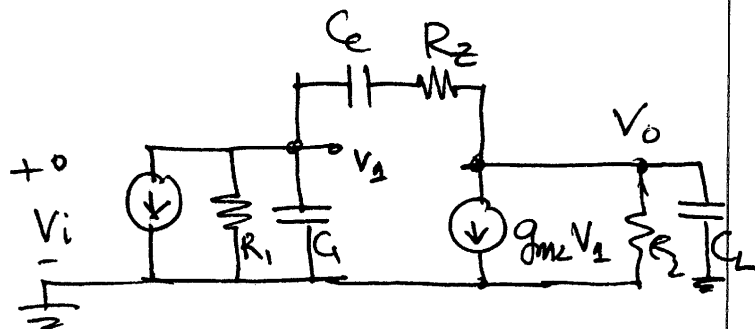


①

AHUJA COMPENSATION

Classic Compensation:

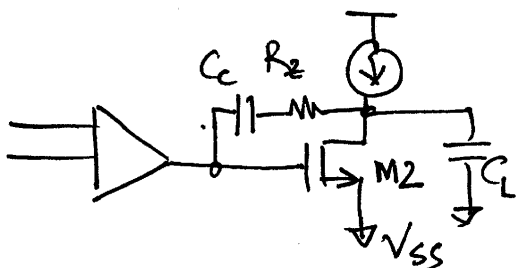

$$P_1 = \frac{1}{(1 + g_{m2}R_2)C_C R_1}$$

$$P_2 = \frac{g_{m2}C_C}{g_{m2}C_L + C_1C_C + C_LC_C} \approx \frac{g_{m2}}{C_L}$$

$$Z_1 = \frac{1}{C_C \left(\frac{1}{g_{m2}} - R_2 \right)}$$


Two issues:

1) Cannot drive large loads.

To be stable: $C_L < \frac{g_{m2}C_C}{g_{m1}}$

2) Poor negative supply rejection.


Intuitive second pole location

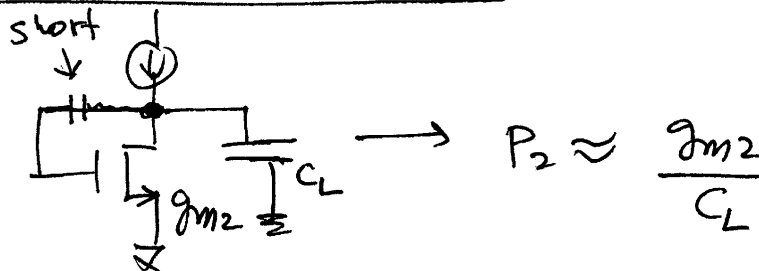

②

Improved Compensation:

Conceptual small signal:

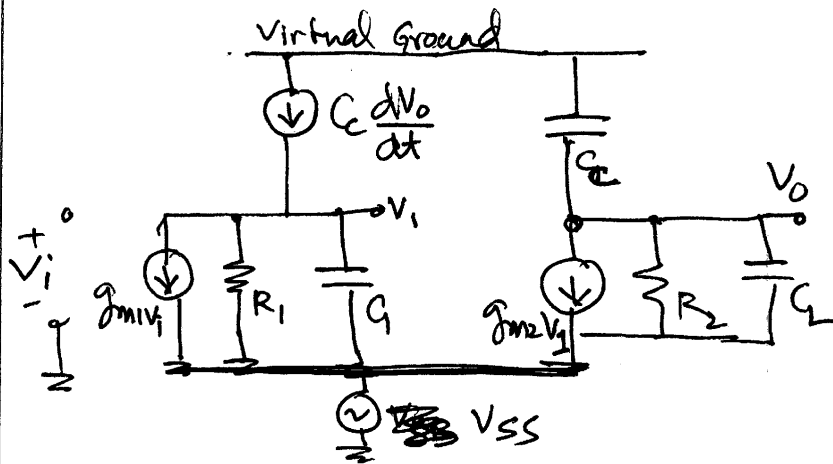

No forward path
so no zero.

$$P_1 \approx \frac{1}{g_{m2}R_2C_cR_1}$$

$$P_2 \approx \frac{g_{m2}C_c}{C_1(C_c + C_L)}$$


Negative PSRR

For open loop:

$$\frac{V_o}{V_{SS}} \approx \frac{1 + sC_1R_1}{(1 + s/P_1)(1 + s/P_2)}$$

For unity gain mode.
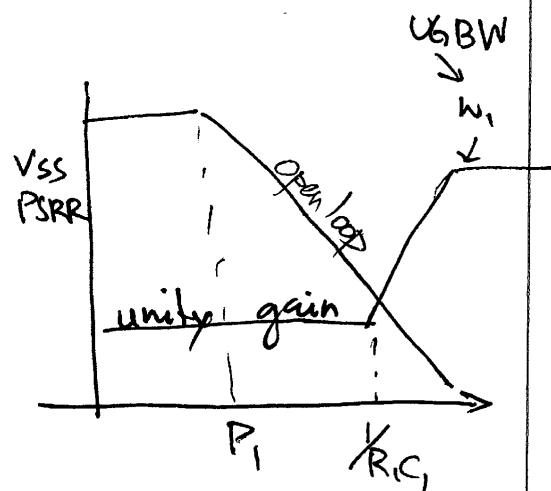
$$\frac{V_o}{V_{SS}} \approx \frac{1 + sC_1R_1}{A_1A_2(1 + s/\omega_1)}$$




Observation:

- * P_1 is the same as before.
- * P_2 moves out $\approx \frac{g_{m2}}{C_1}$
- * No zeros

* V_{SS} PSRR improves by pushing zero to $\frac{1}{R_1C_1}$.

③

Implementation in Class AB Amplifier

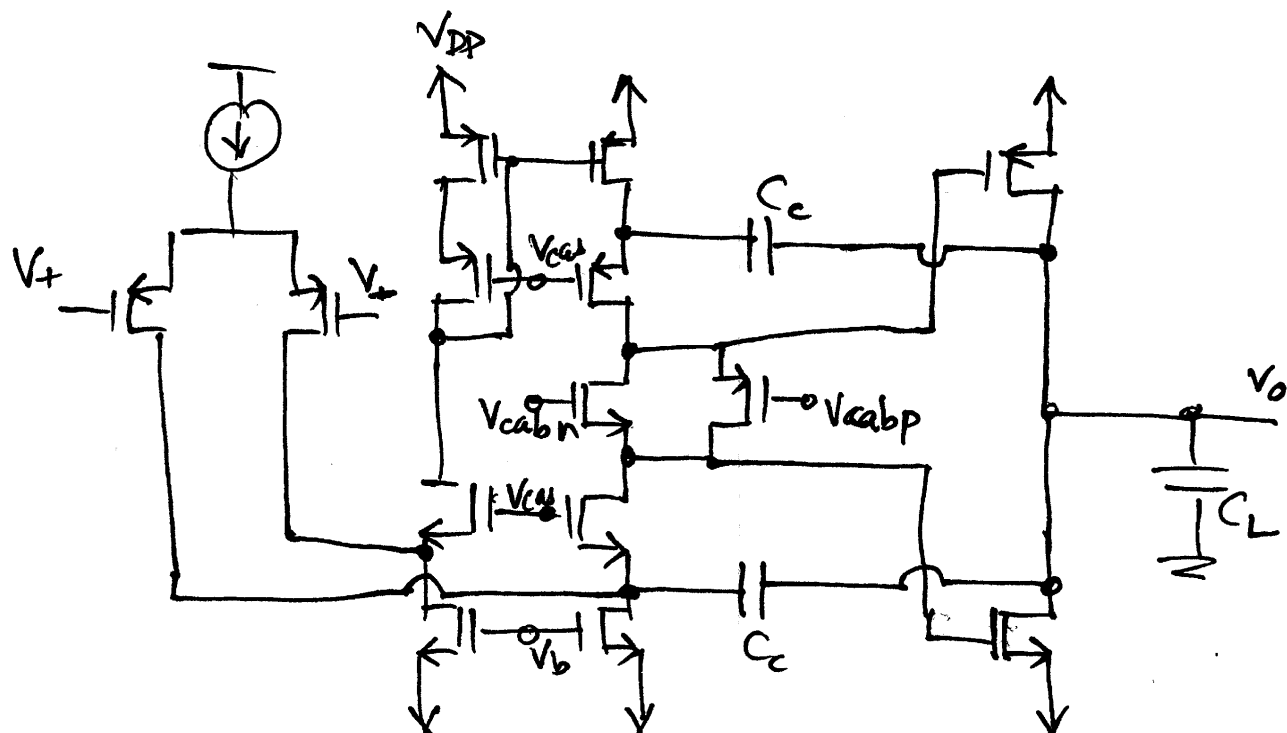

Intuitive way to see the second pole :

Let's simplify by assuming a class A operation.
So the output stage looks like:

